UNIVERSIDAD NACIONAL DE CÓRDOBA

FACULTAD DE MATEMÁTICA ASTRONOMÍA, FÍSICA Y COMPUTACIÓN.

ARQUITECTURA DE COMPUTADORAS

TEÓRICOS: PABLO A. FERREYRA

PRÁCTICOS:
DELFINA VELEZ
AGUSTÍN LAPROVITA
GONZALO VODANOVICK

T2: HARDWARE DESCRIPTION LANGUAGES (A8 Parametrized Modules – N-bit Multiplexers)

Example A.40 Parameterized *N*-bit Multiplexers

```
SystemVerilog  
module mux2
  \#(parameter\ width = 8)
   (input logic [width-1:0] d0, d1,
    input logic
                               s,
    output logic [width-1:0] y);
   assign y = s ? d1 : d0;
endmodule
```


T2: HARDWARE DESCRIPTION LANGUAGES (A8 Parametrized Modules – N-bit Multiplexers)

SystemVerilog (continued) module mux4 8(input logic [7:0] d0, d1, d2, d3, input logic [1:0] s, output logic [7:0] y); logic [7:0] low, hi; mux2 lowmux(d0, d1, s[0], low); mux2 himux(d2, d3, s[0], hi);mux2 outmux(low, hi, s[1], y); endmodule

T2: HARDWARE DESCRIPTION LANGUAGES (A8 Parametrized Modules – N-bit Multiplexers)

```
module mux4 12(input logic [11:0] d0, d1, d2, d3,
               input logic [1:0] s,
               output logic [11:0] y);
  logic [11:0] low, hi;
  mux2 #(12) lowmux(d0, d1, s[0], low);
  mux2 \# (12) himux(d2, d3, s[0], hi);
  mux2 \# (12) outmux(low, hi, s[1], y);
endmodule
```

 T2: HARDWARE DESCRIPTION LANGUAGES (A8 Parametrized Modules - N-bit Multiplexers)



T2: HARDWARE DESCRIPTION LANGUAGES (A8 Parametrized Modules - N-bit Decoder)

Example A.41 Parameterized *N*:2^N Decoder


```
SystemVerilog
module decoder \#(parameter N = 3)
                (input logic [N-1:0] a,
                 output logic [2**N-1:0] y);
  always comb
    begin
      y = 0;
      y[a] = 1;
    end
endmodule
2**N indicates 2N.
```

T2: HARDWARE DESCRIPTION LANGUAGES (A8 Parametrized Modules – N-bit AND remember Reductor Operators)

 Example A.42 Parameterized *N*-input AND Gate

```
SystemVerilog
module andN
  \#(parameter\ width = 8)
   (input logic [width-1:0] a,
    output logic
                              y);
  genvar i;
  logic [width-1:1] x;
  generate
    for (i=1; i<width; i=i+1) begin:forloop
      if (i == 1)
        assign x[1] = a[0] & a[1];
      else
        assign x[i] = a[i] \& x[i-1];
    end
  endgenerate
  assign y = x[width-1];
endmodule
```

T2: HARDWARE DESCRIPTION LANGUAGES (A8 Parametrized Modules N-bit AND remember Reductor Operators)




T2: HARDWARE DESCRIPTION LANGUAGES (A9 Memories – RAM With Separate Din and Dout)

 Example A.43 RAM

SystemVerilog module ram #(parameter N = 6, M = 32)(input logic clk, input logic we, input logic [N-1:0] adr, input logic [M-1:0] din, output logic [M-1:0] dout); logic [M-1:0] mem[2**N-1:0]; always @(posedge clk) if (we) mem[adr] <= din; assign dout = mem[adr]; endmodule

T2: HARDWARE DESCRIPTION LANGUAGES (A9 Memories – RAM With Separate Din and Dout)




T2: HARDWARE DESCRIPTION LANGUAGES (A9 Memories RAM With Bidirectional Data Bus)

 Example A.44 RAM with Bidirectional Data Bus

```
SystemVerilog
module ram \#(parameter N = 6, M = 32)
           (input logic clk,
            input logic we,
            input logic [N-1:0] adr,
            inout tri [M-1:0] data);
  logic [M-1:0] mem[2**N-1:0];
  always @(posedge clk)
    if (we) mem[adr] <= data;
  assign data = we ? 'z : mem[adr];
endmodule
```

T2: HARDWARE DESCRIPTION LANGUAGES (A9 Memories RAM With Bidirectional Data Bus)




T2: HARDWARE DESCRIPTION LANGUAGES (A9 Memories – Three Ported Registers Files)

 Example A.45 Three-Ported Register File

```
SystemVerilog
module ram3port \#(parameter N = 6, M = 32)
                 (input logic clk,
                 input logic we3,
                 input logic [N-1:0] a1, a2, a3,
                 output logic [M-1:0] d1, d2,
                 input logic [M-1:0] d3);
  logic [M-1:0] mem[2**N-1:0];
  always @(posedge clk)
    if (we3) mem[a3] \le d3;
  assign d1 = mem[a1];
  assign d2 = mem[a2];
endmodule
```

T2: HARDWARE DESCRIPTION LANGUAGES (A9 Memories – Three Ported RegistersFiles)



T2: HARDWARE DESCRIPTION LANGUAGES (A9 Memories – ROMs)

Example A.46 ROM

```
SystemVerilog
module rom(input logic [1:0] adr,
           output logic [2:0] dout);
  always comb
    case(adr)
      2'b00: dout = 3'b011;
      2'b01: dout = 3'b110;
      2'b10: dout = 3'b100;
      2'b11: dout = 3'b010;
    endcase
endmodule
```

T2: HARDWARE DESCRIPTION LANGUAGES (A10 Test Benches -Basic Tests)

Example A.47 Testbench

```
SystemVerilog
module testbench1();
 logic a, b, c;
 logic y;
 // instantiate device under test
 sillyfunction dut(a, b, c, y);
 // apply inputs one at a time
 initial begin
   a = 0; b = 0; c = 0; #10;
   c = 1;
                      #10;
   b = 1; c = 0; #10;
   c = 1;
                     #10;
   a = 1; b = 0; c = 0; #10;
   c = 1;
                      #10;
   b = 1; c = 0; #10;
   c = 1;
                      #10;
 end
endmodule
```

T2: HARDWARE DESCRIPTION LANGUAGES (A10 Test

Benches - Self Ch) Example A.48 Self-Checking Testbench

SystemVerilog

```
module testbench2();
  logic a, b, c;
  logic y;
  // instantiate device under test
  sillyfunction dut(a, b, c, y);
  // apply inputs one at a time
  // checking results
  initial begin
    a = 0; b = 0; c = 0; #10;
    assert (y === 1) else $error("000 failed.");
    c = 1;
                         #10;
   assert (y === 0) else $error("001 failed.");
   b = 1; c = 0;
                        #10;
   assert (y === 0) else $error("010 failed.");
    c = 1;
                         #10:
    assert (y === 0) else $error("011 failed.");
    a = 1; b = 0; c = 0; #10;
    assert (y === 1) else $error("100 failed.");
    c = 1;
                         #10:
    assert (y === 1) else $error("101 failed.");
    b = 1; c = 0;
                        #10;
    assert (y === 0) else $error("110 failed.");
```

T2: HARDWARE DESCRIPTION LANGUAGES (A10 Test Benches – Self Checking)

```
assert (y === 0) else $error("010 failed.");
                          #10;
    c = 1;
    assert (y === 0) else $error("011 failed.");
    a = 1; b = 0; c = 0; #10;
    assert (y === 1) else \( \)error("100 failed.");
    c = 1;
                           #10;
    assert (y === 1) else $error("101 failed.");
    b = 1; c = 0; #10;
    assert (y === 0) else $error("110 failed.");
    c = 1;
                          #10;
    assert (y === 0) else \( \frac{\text{"111 failed."}}{\text{;}} \);
  end
endmodule
```

T2: HARDWARE DESCRIPTION LANGUAGES (A10 Test Benches)

Example A.49 Testbench with Test Vector File

SystemVerilog module testbench3(); logic clk, reset; logic a, b, c, yexpected; logic у; logic [31:0] vectornum, errors; logic [3:0] testvectors[10000:0]; // instantiate device under test sillyfunction dut(a, b, c, y); // generate clock always begin clk = 1; #5; clk = 0; #5;end // at start of test, load vectors // and pulse reset

T2: HARDWARE DESCRIPTION LANGUAGES (A10 Test Benches – Automatic File Based)

```
// at start of test, load vectors
// and pulse reset
initial
 begin
    $readmemb("example.tv", testvectors);
   vectornum = 0; errors = 0;
    reset = 1; #27; reset = 0;
 end
// apply test vectors on rising edge of clk
always @(posedge clk)
 begin
    #1; {a, b, c, yexpected} =
          testvectors[vectornum];
 end
```

T2: HARDWARE DESCRIPTION LANGUAGES (A10 Test Benches – Automatic File Based)

SystemVerilog (continued)

```
// check results on falling edge of clk
   always @(negedge clk)
    if (~reset) begin // skip during reset
      if (y !== yexpected) begin
        $display("Error: inputs = %b", {a, b, c});
        $display(" outputs = %b (%b expected)",
                y, yexpected);
        errors = errors + 1;
      end
      vectornum = vectornum + 1;
     if (testvectors[vectornum] === 'bx) begin
        $display("%d tests completed with %d
                 errors", vectornum, errors);
        $finish;
      end
    end
endmodule
```